

O módulo de interface com o *LCD* (*Serial LCD Interface*, *SLCDC*) implementa a receção em série da informação enviada pelo módulo de controlo, entregando-a posteriormente ao *LCD*, conforme representado na Figura 1.

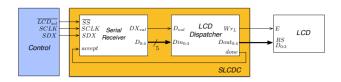


Figura 1 – Diagrama de blocos do Serial LCD Controller

O *SLCDC* recebe em série uma mensagem constituída por cinco bits de informação. A comunicação com o *SLCDC* realiza-se segundo o protocolo ilustrado na Figura 2, tendo como primeiro bit de informação, o bit RS que indica se a mensagem é de controlo ou dados, os restantes bits contêm os dados a transmitir ao *LCD*.

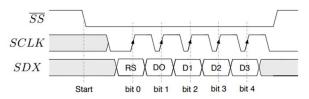


Figura 2 – Protocolo de comunicação com *Serial LCD Controller*

O emissor, realizado em software, quando pretende enviar uma trama para o SLCDC promove uma condição de início de trama (Start), que corresponde a uma transição descendente na linha de \overline{LCD}_{sel} . Após a condição de início, o SLCDC armazena os bits da trama nas transições ascendentes do sinal SCLK.

1 Serial Receiver

O bloco *Serial Receiver* do *SLCDC* é constituído por três blocos principais: i) um bloco de controlo; ii) um contador de bits recebidos; e iii) um bloco conversor série paralelo, designados respetivamente por *Serial Control*, *Counter*, e *Shift Register*. O *Serial Receiver* foi implementado com base no diagrama de blocos apresentado na Figura 3.

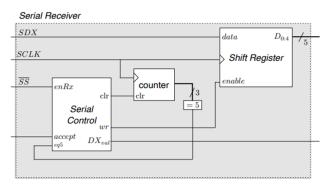


Figura 3 – Diagrama de blocos do Serial Receiver

O bloco *Shift Register* foi implementado de acordo com o diagrama de blocos representado na Figura 4.

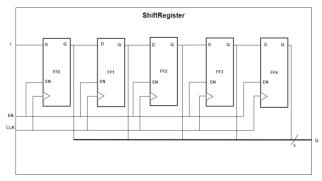


Figura 4 – Diagrama de blocos do Shift Register

Foram utilizados 5 *Flip-Flops* ligados em série. A entrada do primeiro *Flip-Flop* é a entrada *I* do circuito, e os restantes *Flip-Flop* têm como a entrada a saída do *Flip-Flop* anterior. As saídas dos cinco *Flip-Flops* representam o sinal de dados de cinco bits.



O bloco *Serial Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 5.

A descrição hardware do bloco *Serial Receiver* em *VHDL* encontra-se no Anexo A.

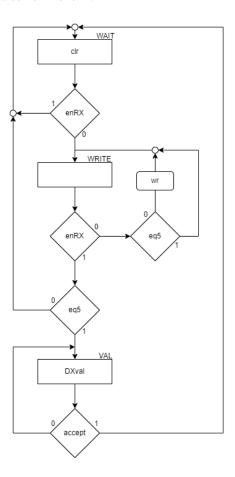


Figura 5 – Máquina de estados do bloco Serial Control

Inicialmente a máquina encontra-se no estado WAIT, em que se limpa o valor do contador e se espera para que o LCD seja selecionado. Quando é selecionado o serial receiver do LCD através de enRX, a máquina passa para o estado **WRITE** em que ativa o *Shift Register* através do sinal *wr* enquanto não são enviados os 5 bits de informação (Figura 2). Assim que são enviados os cinco bits de informação, a máquina desativa o sinal wr e espera para que o LCD deixe de ser selecionado através de enRX para sinalizar que tem dados a enviar ao LCD Dispatcher. Se forem enviados bits de informação insuficientes ou a mais, então a máquina de estados invalida a trama quando o LCD deixa de ser selecionado e volta para o estado WAIT. Caso seja enviada uma trama válida a máquina passa para o estado VAL. Neste estado, envia o sinal DXval para o LCD Dispatcher, para indicar que tem dados a enviar. Quando o sinal accept é enviado pelo LCD Dispatcher a indicar que a trama foi aceite, pode ser iniciado um novo ciclo de escrita e a máquina volta para o estado WAIT.

2 Dispatcher

O bloco *Serial Dispatcher* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 6. A descrição hardware do bloco *Serial Dispatcher* em VHDL encontra-se no Anexo B.

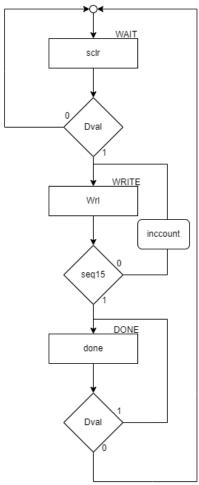


Figura 6 - Máquina de estados do bloco LCD Dispatcher

O bloco *Dispatcher* entrega a trama recebida pelo Serial Receiver ao LCD através da ativação do sinal *WrL*, após este ter recebido uma trama válida, indicado pela ativação do sinal *DXval*.

O *LCD* processa as tramas recebidas de acordo com os comandos definidos pelo fabricante, não sendo necessário esperar pela sua execução para libertar o canal de receção série. Assim, o *Dispatcher* pode sinalizar ao *Serial Receiver* que a trama foi processada, ativando o sinal *done*

Esta implementação de máquina de estados usa um contador de 4 bits para obedecer às especificações do *LCD* (Figura 7).

No estado **WRITE**, em que o sinal de *WrL* está ativo, ou seja, está a ser enviado um sinal High de *Enable* para o *LCD*, incrementa-se o contador até chegar a 15. Quando o contador chega a 15, a máquina de estados passa para o



estado **DONE** em que sinaliza ao *Serial Receiver* que a trama foi processada. Neste estado, a máquina espera até o *Serial Receiver* baixar o sinal *Dval*, e quando o faz, volta para o estado inicial **WAIT** em que se faz reset ao valor do contador. Como cada ciclo de clock na placa DE-10 Lite dura 20 ns (50 MHZ), para o contador chegar a 15 são necessários 300 ns, ou 15 ciclos de clock. Então, a máquina obedece às especificações do *LCD*, que requerem que o sinal de EN esteja ativo pelo menos 230 ns.

Parameter	Symbol	Min (1)	Typ (1)	Max (1)	Unit
Enable Cycle Time	t _c	500	-	-	ns
Enable Pulse Width (High)	t_{w}	230	-	-	ns
Enable Rise/Fall Time	t_r, t_f	-	-	20	ns
Address Setup Time	t _{as}	40	-	-	ns
Address Hold Time	t _{ah}	10	-	-	ns
Data Setup Time	t _{ds}	80	-		ns
Data Hold Time	t _h	10	-	-	ns

Figura 7 – Especificações de ciclo de escrita do LCD

3 Interface com o Control

Implementou-se o módulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura lógica apresentada na Figura 8.



Figura 8 – Diagrama lógico do módulo *Control* de interface com o módulo *SLCDC*

LCD e *Serial Emitter* desenvolvidos são descritos nas secções 3.1 e 3.2, e o código fonte desenvolvido nos Anexos D e E, respetivamente.

3.1 *LCD*

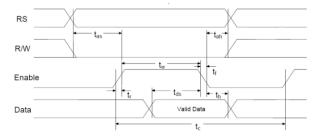


Figura 9 – Diagrama temporal de ciclo de escrita no LCD



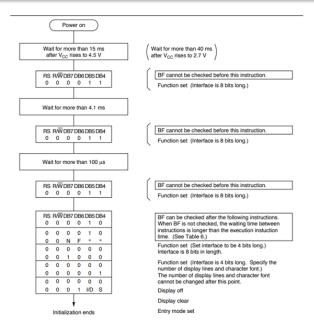


Figura 10 – Sequência de inicialização do LCD

	-	Code										Execution Time (max) (when f or	
Instruction	_	R/W	_		DB5	DB4	DB3	DB2	DB1		Description	f _{osc} is 270 kHz)	
Clear display	0	0	0	0	0	0	0	0	0	1	Clears entire display and sets DDRAM address 0 in address counter.		
Return home	0	0	0	0	0	0	0	0	1	-	Sets DDRAM address 0 in address counter. Also returns display from being shifted to original position. DDRAM contents remain unchanged.	1.52 ms	
Entry mode set	0	0	0	0	0	0	0	1	I/D	S	Sets cursor move direction and specifies display shift. These operations are performed during data write and read.	37 μs	
Display on/off control	0	0	0	0	0	0	1	D	С	В	Sets entire display (D) on/off cursor on/off (C), and blinking of cursor position character (B).	. 37 µ5	
Cursor or display shift	0	0	0	0	0	t:	S/C	R/L	-	-	Moves cursor and shifts display without changing DDRAM contents.	37 μ5	
Function set	0	0	0	0	1	DL	N	F	-	-	Sets interface data length (DL), number of display lines (N), and character font (F).	37 µ5	
Set CGRAM address	0	0	0	1	ACG	ACG	ACG	ACG	ACG	ACC	Sets CGRAM address. CGRAM data is sent and received after this setting.	37 μ5	
Set DDRAM address	0	0	1	ADD	ADD	ADD	ADD	ADD	ADD	ADD	Sets DDRAM address. DDRAM data is sent and received after this setting.	37 µ\$	
Read busy flag & address	0	1	BF	AC	AC	AC	AC	AC	AC	AC	Reads busy flag (BF) indicating internal operation is being performed and reads address counter contents.	0 µs	
Write data to CG or DDRAM	1	0	Write data			Writes data into DDRAM or CGRAM.	37 μs t _{κ00} = 4 μs*						
Read data from CG or DDRAM	1	1	Read	d data							Reads data from DDRAM or CGRAM.	37 μs t ₄₀₀ = 4 μs*	
S/C S/C S/C R/L		= 1: = 0: = 1: = 0: = 1: = 0: = 1: = 1: = 1: = 1:	Decr Accc Disp Curs Shift Shift 8 bit 2 line 5 x 1	ement rement ompani lay shi or mon to the to the s, DL : es, N : 0 dots nally o	right left 0: 4 i 0: 1 perati	bits line 0: 5 x	8 dots				DDRAM: Display data RAM GGRAM: Character generator RAM ACG: CGRAM address ADD: DDRAM address (corresponds to cursor address) AC: Address counter used for both DD and CGRAM addresses	Execution time changes when frequency changes Example: When t_w or t_{osc} is 250 kHz, $37~\mu s \times \frac{270}{250} = 40~\mu t$	

Figura 11 – Lista de comandos do *LCD*

A classe *LCD* é responsável por controlar o ecrã *LCD* em Hardware, através de comunicação serial com interface de 4 bits.

Foram adicionadas as constantes LINES, COLS, RSBITMASK, ENMASK, SERIALMASK, DATAMASK, PULSEDELAY, RISEDELAY, INITDELAY, CMDDELAY, DATA_FRAME E CMD_FRAME.

As constantes LINES e COLS representam as linhas e colunas do LCD, as constantes MASK representam as

posições dos respetivos sinais na *USB Port*, as constantes DELAY representam os tempos de atraso necessários para o funcionamento correto do *LCD* e as constantes FRAME representam as tramas de 5 bits a enviar para o *LCD*.

Também foi utilizada a função global adicional waitTimeNano, que espera um tempo definido em nanossegundos

Foi adicionada a função Pulse(), que realiza um pulso de enable com tempos de espera PULSEDELAY (500 nanosegundos) (ver to na Figura 9) com a utilização de HAL.setBits(), e HAL.clrBits().

A função WriteNibbleParallel(rs: Boolean, data: Int) ativa ou desativa o bit rs do LCD dependendo do valor rs passado como parâmetro (false para comando, true para dados). Após um tempo de espera de 100 nanosegundos (RISEDELAY), envia os dados para o *LCD* e chama a função Pulse(), que escreve os dados no *LCD*.

A função WriteNibbleSerial(rs: Boolean, data: Int) prepara os 5 bits de dados a enviar através do Serial Emitter e envia-os através de SerialEmitter.send(). A trama de cinco bits está representada na Figura 2.

A função WriteNibble(rs: Boolean, data: Int) escreve um nibble em modo paralelo ou serial, dependendo do valor do bit na posição SERIALMASK da *USB Port*. Como apenas vão ser escritos bits em modo serial através do *SLCDC*, esta função apenas envia bits em modo serial e não existe bit atribuído na USB Port para Serial.

A função writeByte(rs : Boolean, data: Int) escreve dois nibbles, chamando a função writeNibble duas vezes. Inicialmente escreve o valor alto de data (bits de data deslocados quatro vezes para a direita) e posteriormente o valor baixo de data (data and 00001111).

A função writeCMD(data: Int) escreve um comando no *LCD*, sendo que chama a função writeByte com o parâmetro rs False, e espera o tempo CMDDELAY(2 milissegundos).

A função writeDATA(data: Int) escreve dados no LCD, sendo que chama a função writeByte com o parâmetro rs True, e depois espera CMDDELAY (2 milissegundos).

A função init() realiza a sequência de inicialização do *LCD* representada na Figura 10, ao utilizar as funções



writeNibble e writeCMD, com os tempos de espera especificados.

A função write(c: Char) escreve no *LCD* o código do caráter passado como parâmetro ao chamar a função writeDATA.

A função write(text: String) escreve no *LCD* uma String ao chamar a função write anterior para cada caráter na String.

A função cursor(line: Int, column: Int) Posiciona o *LCD* ao chamar a função writeCMD com o comando **Set DDRAM address** do *LCD*.

A função clear() Limpa o *LCD* ao chamar a função writeCMD com o comando **Clear Display** do *LCD*

3.2 Serial Emitter

A classe *Serial Emitter* é responsável por envio de dados para o *LCD* ou o controlador da porta em modo serial.

Foram adicionadas as constantes DELAY, SDXMASK, SCLKMASK e BUSYMASK.

As constantes MASK representam as posições dos respetivos sinais na *USB Port*, e a constante DELAY representa o tempo de atraso entre pulsos de SCLK.

Também foi utilizada a função global adicional waitTimeNano, que espera um tempo definido em nanossegundos.

Foi adicionada a função clkPulse(), que realiza um pulso de SCLK com tempos de espera DELAY(100 nanosegundos) ao chamar HAL.setBits(), e HAL.clrBits().

A função init() inicia a classe colocando o sinal SCLK a 0, e desselecionando os *Serial Receivers* da porta e do *LCD*.

A função send(addr: Destination, data: Int) envia os dados serialmente. Inicialmente seleciona um dos *Serial Controllers* através de HAL.writeBits(), e espera um tempo DELAY(100 nanosegundos) para o hardware preparar a escrita. Após o tempo DELAY são escritos os bits da trama de dados um a um através de HAL.writeBits() de acordo com a Figura 2, sendo que para cada um deles é chamada a função clkPulse().

A função isbusy() verifica se o canal série está ocupado, utilizando a função HAL.isBit() para verificar o mesmo.

4 Conclusões

Neste módulo foi implementado o módulo *Serial LCD Controller* através dos blocos *Serial Receiver* e *LCD Dispatcher*, que implementa a receção em série da informação enviada pelo módulo de controlo, entregando-a posteriormente ao *LCD*.

Os blocos *Serial Control* e *LCD Dispatcher* operam com a frequência da placa DE-10 Lite da Intel (50 MHz), ou um ciclo a cada 20 nanosegundos.

A máquina de estados do *LCD Dispatcher* irá gastar 20 nanosegundos no primeiro estado com *wrL* desativado assumindo que *Dval* está ativo, 320 nanosegundos no segundo estado com *wrL* ativado, e no último estado o tempo para o *Serial Receiver* baixar *Dval* com *done* ativado e *wrL* desativado.

Para enviar 5 bits de informação, O Serial Receiver demora 20 ns depois de ser selecionado o Serial Controller do LCD a passar para o segundo estado. Neste segundo estado, o circuito demora o tempo do software a enviar os 5 bits de informação através de ciclos de SCLK e ativar o sinal SS. No terceiro estado, a máquina demora o tempo do LCD Dispatcher enviar os dados e ativar o sinal Done (340 nanosegundos) mais 20 nanosegundos quando Done é ativado.

Em termos de recursos da placa DE-10 Lite, na implementação do *Serial LCD Control* foram utilizados 23/49670 elementos lógicos (0,05%), 16 registos, e 11/360 pinos (3%).



A. Descrição VHDL do bloco Serial Receiver

```
LIBRARY ieee;
USE ieee.std logic 1164.all;
ENTITY SerialReceiver is
PORT (busy: out std logic;
            SDX : in STD LOGIC;
            SCLK : in STD LOGIC;
            SS: in std logic;
            accept : IN STD LOGIC;
            clk: IN std logic;
            D : out std_logic_vector(4 downto 0);
            DXval : out STD LOGIC;
            RST: in std logic
            );
end SerialReceiver;
ARCHITECTURE logic OF SerialReceiver is
component SerialControl is
      port (
            RST : in std logic;
            clk : in std logic;
            enRX : in std logic;
            accept: in std logic;
            eq5 : in std logic;
            clr : out std logic;
            wr : out std logic;
            DXval : out std logic
      );
end component;
component counterUp3 is
PORT (
            RST : in STD LOGIC;
            CE: in std \overline{logic};
            CLK : IN STD LOGIC;
            Q : out std \overline{\text{logic}} vector(2 downto 0)
            );
end component;
component Shiftregister is
PORT( I : in std logic;
            EN : in STD LOGIC;
            RST : in std logic;
            CLK : IN STD LOGIC;
            DATA: out std logic vector(4 downto 0)
end component;
signal sclr, swr, seq5, sval: std_logic;
signal scounter : std_logic_vector ( 2 downto 0);
```



Begin

```
Control : SerialControl port map(
      RST => RST,
      clk => clk,
      enRX => SS,
      accept => accept,
      eq5 => seq5,
      clr => sclr,
      wr => swr,
      DXval => sval
);
Counter: counterUp3 port map(
      RST => sclr,
      CE => '1',
      CLK => SCLK,
      Q => scounter
);
SRegister : Shiftregister port map(
      I \Rightarrow SDX,
      EN => swr,
      RST => RST,
      CLK => SCLK,
      DATA => D
);
busy <= sval;</pre>
DXval <= sval;
seq5 <= scounter(0) and not scounter(1) and scounter(2) and not sclk;</pre>
end logic;
```



B. Descrição VHDL do bloco LCD Dispatcher

```
LIBRARY IEEE;
use IEEE.std logic 1164.all;
entity LCD Dispatcher is
      port (
            clk : in std logic;
            RST : in std logic;
            Dval: in std logic;
            Din : in std_logic_vector ( 4 downto 0);
            WrL : out std logic;
            Dout : out std_logic_vector (4 downto 0);
            done : out std logic
      );
end LCD Dispatcher;
architecture logic of LCD Dispatcher is
component counterUp4 is
PORT (
            RST : in STD LOGIC;
            CE : in std \overline{logic};
            CLK : IN STD LOGIC;
            Q : out std \overline{\text{logic vector}} (3 downto 0)
            );
end component;
type STATE TYPE is (STATE WRITE, STATE DONE, STATE WAIT);
signal currentstate, nextstate: STATE TYPE;
signal inccount: std logic;
signal seq15 : std_logic;
signal scount: std logic vector(3 downto 0);
signal sclr: std logic;
begin
      counter: counterUp4 port map(
            clk => clk,
            CE => inccount,
            RST => sclr,
            Q => scount
            );
      currentstate <= STATE WAIT when RST = '1' else nextstate when
rising edge(clk);
      GenerateNextState:
      process(currentstate, Dval, seq15)
            Begin
            case currentstate is
                  when STATE WAIT
                                     => if(Dval = '1') then
```




end logic;

```
nextstate <= STATE WRITE;</pre>
                                     else
                                           nextstate <= STATE WAIT;</pre>
                                     end if;
            when STATE WRITE => if(seq15 = '0') then
                                           nextstate <= STATE WRITE;</pre>
                                           nextstate <= STATE DONE;</pre>
                                     end if;
            WHEN STATE DONE =>
                                    if(Dval = '1') then
                                     nextstate <= STATE DONE;</pre>
                                       nextstate <= STATE WAIT;</pre>
                                     end if;
      end case;
end process;
sclr <= '1' when currentstate = STATE WAIT else '0';</pre>
seq15 <= scount(3) and scount(2) and scount(1) and scount(0);</pre>
inccount <= '1' when currentstate = STATE WRITE and seq15 = '0' else '0';
done <= '1' when currentstate = STATE DONE else '0';
WrL <= '1' when currentstate = STATE WRITE else '0';
Dout <= Din;
```



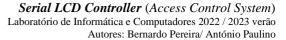C. Atribuição de pinos do módulo SLCDC

```
#-----
# Altera DE10-Lite board settings
#-----
set global assignment -name FAMILY "MAX 10 FPGA"
set_global_assignment -name DEVICE 10M50DAF484C6GES
set_global_assignment -name TOP_LEVEL_ENTITY "DE10_Lite"
set_global_assignment -name DEVICE_FILTER_PACKAGE FBGA
set_global_assignment -name SDC_FILE DE10_Lite.sdc
set global assignment -name INTERNAL FLASH UPDATE MODE "SINGLE IMAGE WITH ERAM"
#-----
# CLOCK
#----
#set instance assignment -name IO STANDARD "3.3-V LVTTL" -to CLOCK 50
#set_instance_assignment -name IO_STANDARD "3.3-V LVTTL" -to CLOCK2 50
#set instance assignment -name IO STANDARD "3.3-V LVTTL" -to CLOCK ADC 10
set location assignment PIN P11 -to clk
#set location assignment PIN N14 -to CLOCK2 50
#set location assignment PIN N5 -to CLOCK ADC 10
#-----
#-----
set_location_assignment PIN C10 -to LCDsel
set location assignment PIN C11 -to SCLK
set location assignment PIN D12 -to SDX
#set location assignment PIN C12 -to SW[3]
#set_location_assignment PIN_A12 -to SW[4]
#set_location_assignment PIN_B12 -to SW[5]
#set location assignment PIN A13 -to SW[6]
#set_location_assignment PIN_A14 -to SW[7]
#set location assignment PIN B14 -to SW[8]
set location assignment PIN F15 -to RST
#-----
# Keyboard
#-----
#set_location_assignment PIN_AA14 -to KEYPAD_LIN[1]
#set location_assignment PIN_W12 -to KEYPAD_LIN[2]
#set_location_assignment PIN_AB12 -to KEYPAD LIN[3]
#set location assignment PIN AB11  -to KEYPAD COL[0]
#set_location_assignment PIN_AB10 -to KEYPAD COL[1]
#set location assignment PIN AA8 -to KEYPAD COL[3]
#-----
# LCD
#-----
set_location_assignment PIN_W8
set_location_assignment PIN_V5
                          -to D[0]
                         -to E
#set location assignment PIN AA15   -to Data LCD[0]
#set_location_assignment PIN_W13 -to Data_LCD[1]
#set location assignment PIN AB13 -to Data LCD[2]
#set_location_assignment PIN_Y11 -to Data_LCD[3]
set_location_assignment PIN_W11 -to D[1]
```







D. Código Kotlin - LCD

```
* 22/5/2023
* Manages the LCD for the [AccessControlSystem], using 4-bit interface.
* @property LINES the number of lines on the LCD
* @property COLS the number of columns on the LCD
* @author Bernardo Pereira
* @author António Paulino
* @see SerialEmitter
* @see HAL
object LCD {
   const val LINES = 2
   const val COLS = 16
    /**
     * The bit mask of the RS output on the USB output port
   private const val RS BIT MASK = 0b00010000
    /**
    ^{\star} The bit mask of the EN output on the USB output port
   private const val EN MASK = 0b00100000
    /**
    ^{\star} The bit mask of the Data input on the USB input port
   private const val DATA MASK = 0b00001111
    * The delay in nanoseconds between EN pulses to the LCD
   private const val PULSE DELAY = 500
    /**
     * The delay in nanoseconds for the rise time of the bit signals.
   private const val RISE DELAY = 100
    /**
    * The delay between LCD initialization commands
   private const val INIT DELAY = 30
    * The delay in milliseconds between LCD commands.
   private const val CMD DELAY = 2
```



```
* A nibble with the RS bit set to 0, to send a command to the LCD
   private const val CMD FRAME = 0b00000
    /**
    * A nibble with the RS bit set to 1, to send data to the LCD
   private const val DATA FRAME = 0b00001
    /**
     * Sends an EN pulse to the LCD
   private fun pulse() {
        waitTimeNano(PULSE DELAY)
        HAL.setBits(EN MASK)
        waitTimeNano(PULSE DELAY)
        HAL.clrBits(EN MASK)
        waitTimeNano(PULSE DELAY)
    }
    /**
     * Sends a command or data nibble (4 bits) to the LCD in parallel mode.
     * @param rs Defines whether to send a command (false) or data (true)
     * @param data Data to send
   private fun writeNibbleParallel(rs: Boolean, data: Int) {
        if (!rs) {
            HAL.clrBits(RS BIT MASK)
            waitTimeNano(RISE DELAY)
        } else {
            HAL.setBits(RS BIT MASK)
            waitTimeNano(RISE DELAY)
        HAL.writeBits(DATA MASK, data)
        pulse()
    }
    /**
     * Writes a command or data nibble (4 bits) to the LCD in serial mode.
     * @param rs Defines whether to send a command (false) or data (true)
     * @param data Data to send
   private fun writeNibbleSerial(rs: Boolean, data: Int) {
       val datasend = if (rs) DATA FRAME or data.shl(1) else CMD FRAME or
data.shl(1)
       SerialEmitter.send(SerialEmitter.Destination.LCD, datasend)
    }
    /**
    * Writes a command or data nibble (4 bits) to the LCD.
     * @param rs Defines whether to send a command (false) or data (true)
    * @param data Data to send
     */
   private fun writeNibble(rs: Boolean, data: Int) {
```



```
// if (HAL.isBit(SERIALMASK)) {
              writeNibbleSerial(rs, data)h
        //
        // } else {
        // writeNibbleParallel(rs, data)
       // }
       writeNibbleSerial(rs, data)
    }
    /**
    * Writes a command or data byte (8 bits) to the LCD by calling
[writeNibble] two times. One for the 4 high bits
     * and another for the 4 low bits.
    * The 4 High bits must be sent before the 4 Low bits according to the LCD
specifications.
     * @param rs Defines whether to send a command (false) or data (true)
     * @param data Data to send
   private fun writeByte(rs: Boolean, data: Int) {
       val dataHigh = data.shr(4) // 4 high bits
       val dataLow = data.and(0b00001111) // 4 low bits
       writeNibble(rs, dataHigh)
       writeNibble(rs, dataLow)
    }
    * Writes a command to the LCD by calling [writeByte] with the RS flag set
     * @param data Command data to send
   private fun writeCMD(data: Int) {
       writeByte(false, data)
       waitTimeMilli(CMD DELAY)
    }
    /**
    * Writes data to the LCD by calling [writeByte] with the RS flag set to
true.
    * @param data Data to be sent
   private fun writeDATA(data: Int) {
      writeByte(true, data)
    }
    * Initializes the LCD for 4 bit communication mode by following the
specified LCD initialization sequence.
     * Uses the Function set, Display Control, and Entry Mode set commands.
     * Calls the [writeNibble] and [writeCMD] functions.
```



```
fun init() {
        waitTimeMilli(INIT DELAY)
        writeNibble(false, 0b00000011)
        waitTimeMilli(INIT DELAY)
        writeNibble(false, 0b00000011)
        waitTimeMilli(INIT DELAY)
        writeNibble(false, 0b00000011)
        waitTimeMilli(INIT DELAY)
        writeNibble(false, 0b00000010)
        writeCMD(0b00101000) // function set: 4-bit mode, 2 lines, 5x8 dots
        writeCMD(0b00001000) // display control : display off, cursor off, blink
off
        writeCMD(0b00000001) // clear
        writeCMD(0b00000110) // entry mode set: increment cursor, no display
shift
        writeCMD(0b00001100) // display control: display on, cursor off, blink
off
   }
    /**
     * Writes a character to the LCD.
    fun write(c: Char) = writeDATA(c.code)
    /**
    * Writes a string to the LCD.
    * /
    fun write(text: String) {
        for (char in text) {
            write(char)
    }
     * Positions the cursor on the LCD by using the Write data to CG or DDRAM
command.
     * The 7th bit indicates the line position, and the 4 low bits indicate the
column position.
     * @param line the line position for the cursor, 1 for the first line, 2 for
the second line
    * @param column the column position for the cursor, 1 for the first column,
16 for the last column
     */
    fun cursor(line: Int, column: Int) = writeCMD(0b10000000 or (((line - 1) shl
(6)) + column - 1)
    /**
     * Clears the LCD by using the Clear display command.
    */
    fun clear() = writeCMD(0b0000001)
```



}

E. Código Kotlin – SerialEmitter

```
import SerialEmitter.Destination
fun main() {
   HAL.init()
   SerialEmitter.send(Destination.LCD, 0x15)
}
/**
* 22/5/2023
* Serial emitter for sending data to the door controller or the LCD of the
[AccessControlSystem]
* @property Destination Serial emitter destinations.
* @author Bernardo Pereira
* @author António Paulino
* @see LCD
* @see DoorMechanism
* @see HAL
*/
object SerialEmitter {
   enum class Destination(val mask: Int) { LCD(0b00000010), DOOR(0b00000100) }
    * The wait time in nanoseconds between sending bit signals to the hardware
   private const val DELAY = 1000
    /**
    * The bit mask of the SDX output to the USB Port
   private const val SDXMASK = 0b00000001
    /**
    * The bit mask of the SCLK output to the USB Port
   private const val SCLKMASK = 0b10000000
    * The bit mask of the BUSY input on the USB Port. Represents if the serial
receiver is busy.
    */
   private const val BUSYMASK = 0b00100000
    /**
    * The size in bits of frames sent through the serial emitter.
   private const val FRAME_SIZE = 5
```



```
* Initializes the Door Mechanism Control and LCD Serial Receivers by
deselecting them. Sets [isbusy] to false.
     * /
    fun init() {
        HAL.setBits(Destination.LCD.mask)
        HAL.setBits(Destination.DOOR.mask)
        HAL.clrBits(SCLKMASK)
        waitTimeNano(DELAY)
    }
    /**
     * Sends an SCLK pulse to the hardware through the USB Port output port
     * /
   private fun clkPulse() {
        waitTimeNano(DELAY)
        HAL.setBits(SCLKMASK)
        waitTimeNano(DELAY)
        HAL.clrBits(SCLKMASK)
        waitTimeNano(DELAY)
    }
    /**
     * Sends data to the destination Serial Receiver according to the serial
communication protocol for the [AccessControlSystem]
    * @param addr The destination
     * @param data The data to send
     * /
    fun send(addr: Destination, data: Int) {
        HAL.clrBits(addr.mask) //Select the destination Serial Receiver
        waitTimeNano(DELAY)
        for (i in 0 until FRAME SIZE) { //Write frame to LCD
            val sdx = (1.shl(i) and data).shr(i)
            HAL.writeBits(SDXMASK, sdx)
            clkPulse()
        }
        HAL.setBits(addr.mask) //Deselect the destination Serial Receiver
        if (addr == Destination.DOOR) {
            while (!DoorMechanism.finished()) {
                waitTimeMilli(DELAY / 10)
            }
        }
        waitTimeNano(DELAY)
    }
     * Checks if the Door Serial Receiver is busy
```





}

* @return true if the Door Serial Receiver is busy, false otherwise
*/
fun isBusy(): Boolean = HAL.isBit(BUSYMASK)